

## **Basic of isolated power device pre-driver (TLP5231 Operation and Protective Function Setting)**

### **Overview**


This document describes the basics of isolated power device pre-driver TLP5231, a type of gate driver for power MOSFET and IGBT gate control. Gate drivers can be broadly divided into single-function driver and multi-function driver. Those two kinds of driver also drive power device directly and via buffers. The types via buffers are called pre-drivers. This document describes the basics of operation and protective functions unique to pre-driver TLP5231, which has dual-outputs.

### Contents

|                                                                                        |           |
|----------------------------------------------------------------------------------------|-----------|
| <b>1. Overview .....</b>                                                               | <b>3</b>  |
| <b>2. Application .....</b>                                                            | <b>3</b>  |
| 2.1. Application Examples .....                                                        | 3         |
| 2.2. Example of Inverter Applications .....                                            | 3         |
| <b>3. Functional Classification of Gate Drivers .....</b>                              | <b>3</b>  |
| <b>4. Protection Function of Isolated Power Device Pre-driver .....</b>                | <b>5</b>  |
| 4.1. Overcurrent DESAT Detection Method.....                                           | 5         |
| 4.2. Operation of Detecting DESAT (de saturation) .....                                | 6         |
| 4.3. Operation of Blanking Capacitor ( $C_{BLANK}$ ).....                              | 7         |
| 4.4. UVLO Function (Under Voltage Lock Out: Under voltage malfunction prevented) ..... | 8         |
| <b>5. Features of Pre-driver TLP5231.....</b>                                          | <b>9</b>  |
| 5.1. Outline of TLP5231 and Example of Application Circuit .....                       | 9         |
| 5.2. Comparison of TLP5231 and Single-Function Gate Driver Internal Structure .....    | 12        |
| 5.3. Derating of Dead-time Design .....                                                | 12        |
| 5.4. Protective Design (improved flexibility of soft turn-off design).....             | 13        |
| 5.5. Protection Design (fault signal auto-reset) .....                                 | 13        |
| <b>6. Example of Circuit Design Using TLP5231.....</b>                                 | <b>14</b> |
| 6.1. Example of Inverter Application Circuit .....                                     | 14        |
| 6.2. Selection of external MOSFET.....                                                 | 16        |
| 6.3. Selection of MOSFET for Soft Turn-off and Setting of Soft Turn-off Time .....     | 17        |
| 6.4. Setting the blanking capacitor charge current and DESAT detect voltage.....       | 18        |
| 6.5. Setting the Blanking Capacitor ( $C_{BLANK}$ ) .....                              | 18        |
| <b>7. Example of Operation Waveforms Using TLP5231 .....</b>                           | <b>19</b> |
| <b>Changelog.....</b>                                                                  | <b>25</b> |
| <b>Precautions for handling the product .....</b>                                      | <b>26</b> |




is used for the low voltage MOSFET of 100V or less or MOSFET of 200 to 300V, the high withstanding voltage MOSFET of 600V needs the non-isolated or isolated type. Much higher voltage, for example, 1200V withstanding voltage IGBT needs the isolated type.

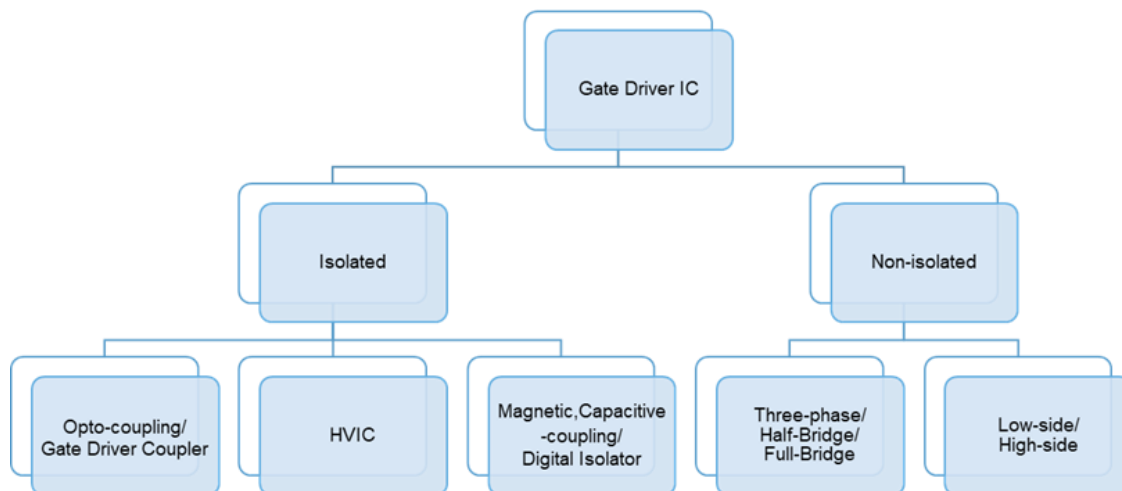


**Fig. 3.1 Gate Driver Types**

In applications requiring isolation, it is possible to drive the power device using a non-isolated gate driver IC, but a separate isolator is required to provide isolation. This means that there is an additional semiconductor component between the controller IC and the power device.

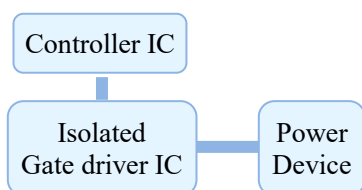

**Fig. 3.2 When Using Isolated Gate Driver ICs**

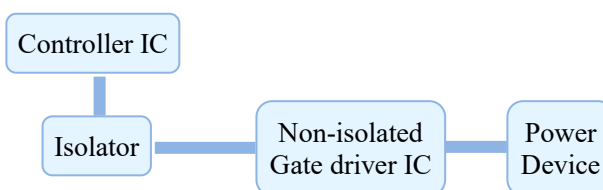

**Fig. 3.3 When Using Non-Isolated Gate Driver ICs**

Gate driver couplers are isolated gate driver ICs used mainly in combination with a power MOSFET of 600V withstand voltage and an IGBT of 1200V withstand voltage because of their high insulation performance and ease of use. Although the isolation voltage is slightly lower, some high-voltage ICs are electrically isolated inside the chip. They are also used in conjunction with high-voltage MOSFET of 600V or IGBT of 1200V withstand voltage. In recent years, digital isolator-type gate driver ICs with magnetic and capacitive insulation are also commercialized, which have the same performance as optical isolation.

This application note deals with opto-isolated gate driver couplers. The structural differences between single-function and smart gate driver-coupler are written in section 5.2, [\(Link\)](#).

### 4. Protection Function of Isolated Power Device Pre-driver

As outlined, the Isolated Power Device Pre-Driver TLP5231 is a similar category of Smart Gate Driver Coupler with built-in power device protection. This section explains the general protection functions.

#### 4.1. Overcurrent DESAT Detection Method

Inverter circuits, the main application of gate driver couplers, usually consist of three rows of two stages, top and bottom, and a total of six gate driver couplers are used. If the upper and lower power devices arranged in series are turned on at the same time due to some trouble, as shown in Fig. 4.1, a high-voltage power supply of several 100V will be short-circuited. This abnormal situation is generally called “arm short”, and a large current of several 100A or more may flow and cause smoking, ignition, or destruction.

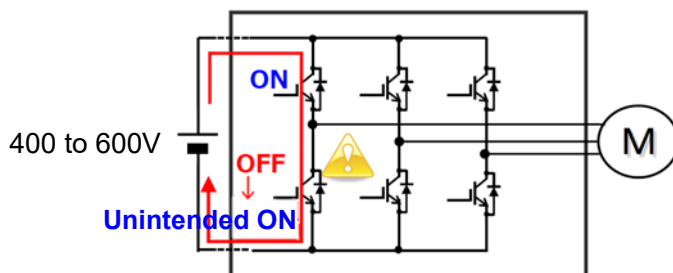


Fig. 4.1 Arm Short Fault in Inverter Circuit

Protecting power devices that handle high voltages and large currents from over currents caused by short-circuit anomalies is very important from the viewpoint of preventing smoking, ignition, and breakage.

The short-circuit tolerance is the time from when an overcurrent flows until the flow destroys the power device. It is necessary to shut off the overcurrent within the short-circuit tolerance.

Although the short-circuit tolerance varies depending on the power device, recent advances in embedding process shrink in power device have resulted in an increasing number of examples requiring protection in a short time to shut off the overcurrent within 1 to 5μs.

The isolated power device pre-driver has an over-current protection function that detects abnormality by monitoring the voltage of the power device that increases in conjunction with the current when an excessive current flows due to some irregularity in the power device, and stops the operation of the power device.

As shown in Fig. 4.2, the voltage across the collector-emitter of IGBT and drain-source of MOSFET is monitored via a high-voltage diode. The voltage drop across the monitored power device is used to estimate the current by converting the I-V static curve of the power device. For this estimation,  $I_C$ - $V_{CE}$  curve or  $I_D$ - $V_{DS}$  curve of the power device is mandatory.

To monitor the collector or drain terminals directly, definitely needs to insert a high reverse withstand voltage fast recovery diode of several 100V or 1000V or higher. This method is called DESAT (de saturation) detection method, and it is difficult to directly monitor the current, but it has the advantage of being relatively simple and inexpensive to compose.

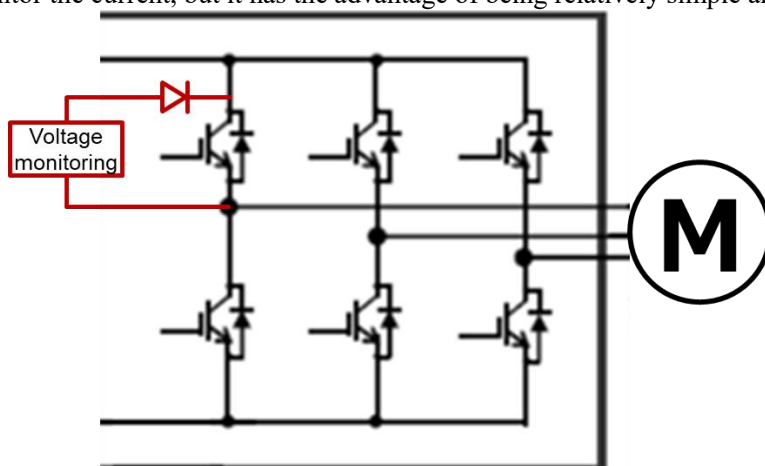


Fig. 4.2 Image of  $V_{CE(sat)}$  DESAT Detection Method Current Monitor

### 4.2. Operation of Detecting DESAT (de saturation)

Fig. 4.3 shows the sequence of protection operation when DESAT is detected, taking TLP5231 as an example.

- ① Overcurrent occurs in the power device (here IGBT).
- ②  $V_{CE(sat)}$  rises in response to overcurrent, and protective operation starts when DESAT threshold voltage exceeds 7.5V (min).
- ③ Turn on external MOSFET for soft turn-off to slowly discharge gate of IGBT and turn off IGBT.
- ④ Transmits error (FAULT) signal to controller IC.

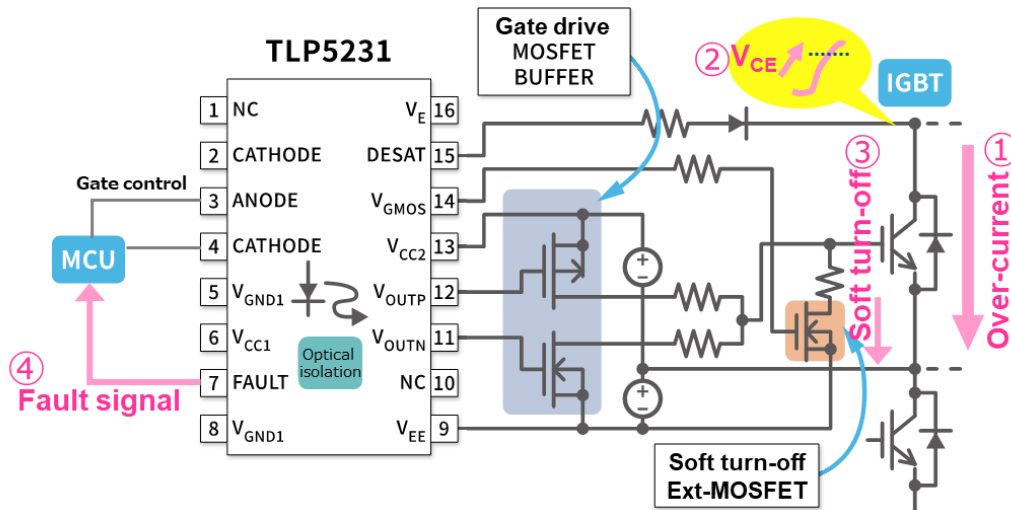


Fig. 4.3 Sequence of protective operation when DESAT is detected

The operation of DESAT detection is described below.

Fig. 4.4 shows the looping of the current that monitors DESAT.

When IGBT is turned on normally and the collector current is applied, DESAT terminal outputs the blanking capacitor charging current  $I_{CHG}$  as a constant current source and superimposes the monitoring current between the collector and emitter of IGBT through the resistor  $R_{DESAT}$  and the high reverse withstand voltage diode  $D_{DESAT}$ .

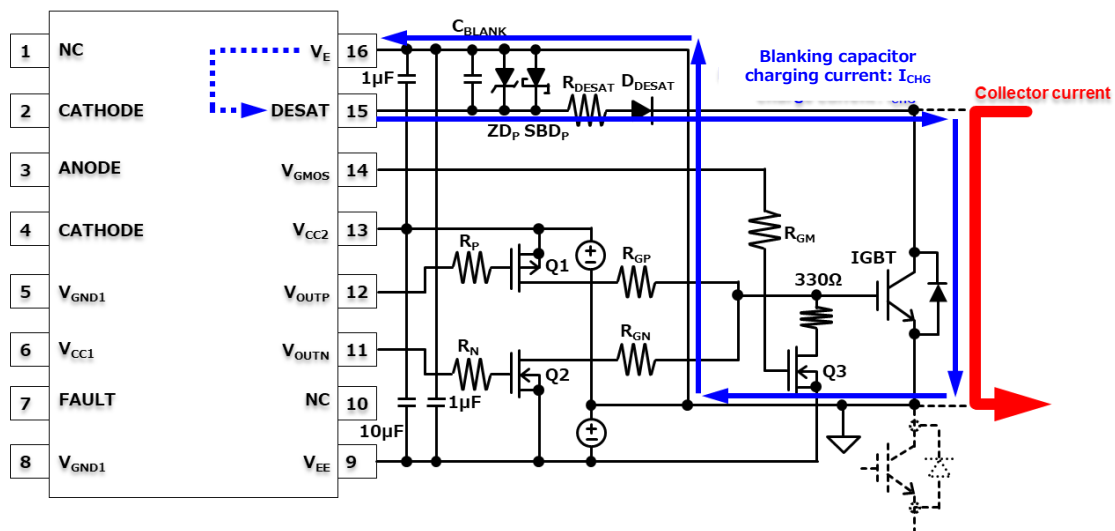


Fig. 4.4 Operation of DESAT Detecting Method

For  $D_{DESAT}$ ,  $I_{CHG}$  is the only forward current that can flow, so a low-capacity (around 100mA) diode is sufficient. However, you should select a low-junction-capacitance diode with a reverse withstand voltage that is high enough than IGBT collector-emitter voltage ( $V_{CES}$ ) and to prevent false positives. When diodes are placed in series, the junction-capacitance becomes the inverse of the number in series, which is effective from the viewpoint of junction-capacitance reduction. However, the reverse withstand voltage when IGBT is turned off may not be applied evenly to diodes in series due to variations in the leakage current of individual diodes. Therefore, you must have a diode with a higher reverse withstand voltage than  $V_{CES}$  of IGBT.

### 4.3. Operation of Blanking Capacitor ( $C_{BLANK}$ )

The previous section explains that the presence or absence of overcurrent can be detected by outputting the blanking capacitor charging current ( $I_{CHG}$ ) from DESAT terminal and monitoring  $V_{ce}$  of IGBT. This section describes the points that must be taken into consideration when designing the overcurrent detection circuit.

DESAT terminal is connected to the collector terminal of IGBT through a high withstand voltage diode ( $D_{DESAT}$ ). If IGBT collector voltage fluctuates due to external noise when IGBT is ON, DESAT voltage may fluctuate through the junction capacitance of  $D_{DESAT}$ . If this DESAT voltage fluctuation exceeds DESAT threshold (8.0V typical), protective operation starts and IGBT is softly turned off. Although DESAT terminals of TOSHIBA's smart gate driver couplers, including TLP5231, are equipped with noise filters, the noise generated by the high-voltage inverter circuit tends to become large, so we recommend that a blanking capacitor ( $C_{BLANK}$ ) shown in Fig. 4.5 be added to form a low-pass filter.

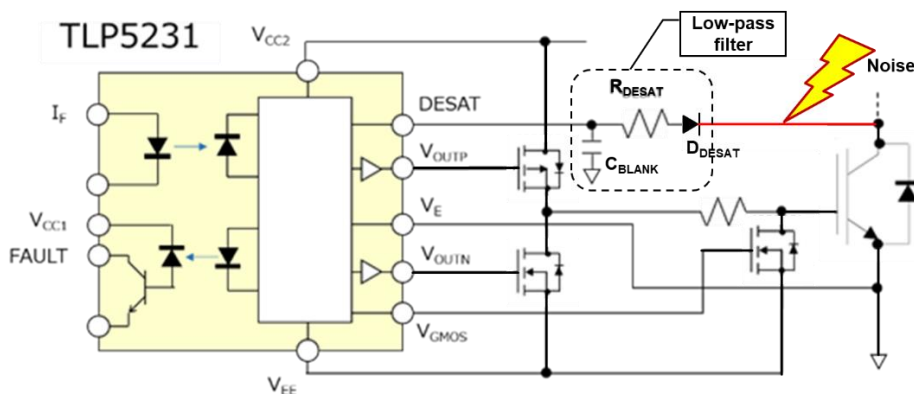


Fig. 4.5 Noise filter configuration by adding DESAT Capacitor ( $C_{BLANK}$ )

As a tradeoff from adding this  $C_{BLANK}$ , there is a delay when  $V_{CE(SAT)}$  reaches DESAT threshold voltage in the event of a short-circuit failure.

Assuming that the time from the occurrence of a short circuit to DESAT threshold voltage is the blanking time ( $t_{BLANK}$ ), the current-voltage operation image of the smart gate driver coupler and IGBT is as shown in Fig. 4.6.

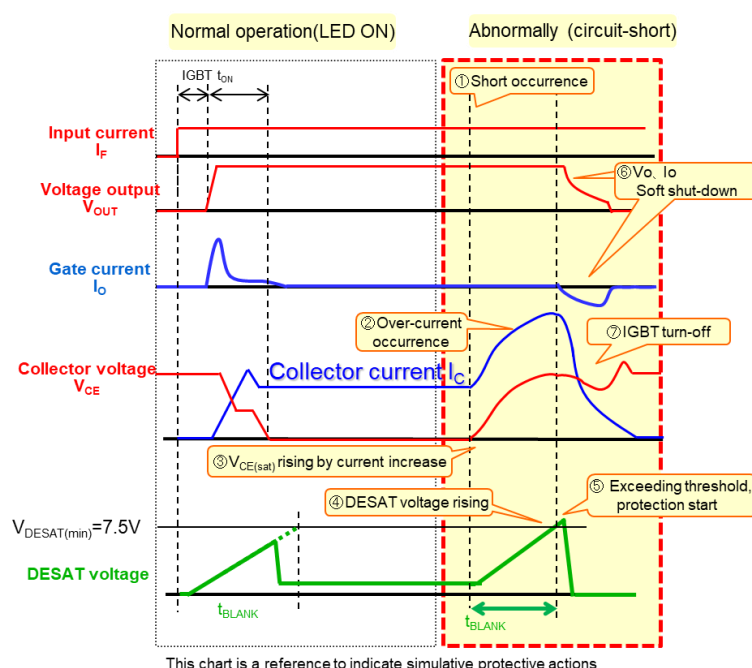


Fig. 4.6 Timing Chart Image of IGBT and Smart Gate Driver Coupler in Case of Short Circuit

If IGBT's  $V_{CE(SAT)}$  spikes due to an overcurrent caused by a short-circuit, it will exceed the power supply voltage of the constant current source and  $I_{CHG}$  will not flow to the IGBT.

Since the current loop is interrupted, DESAT terminal voltage rises toward the open voltage in a short time, and the protection starts beyond the threshold voltage. At this time, if there is a  $C_{BLANK}$ ,  $I_{CHG}$  lost in the destination will flow, and delay will happen for the time to charge the  $C_{BLANK}$ .

#### 4.4. UVLO Function (Under Voltage Lock Out: Under voltage malfunction prevented)

This function monitors the voltage of the gate power supply. When the voltage falls below the operating threshold voltage UVLO threshold ( $V_{UVLO}$ ) set for each driver coupler,  $V_O$  or  $V_{OUT}$  terminal is fixed at a low level and the gate output is shut off as shown in Fig. 4.7.

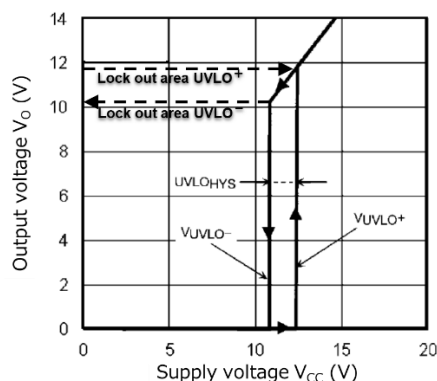


Fig. 4.7 UVLO Operation of Gate Driver Coupler

This is a function to prevent the power device from passing current between the collector and emitter or between the drain and source with insufficient gate voltage, and is intended to prevent damage from overheating. In particular, the power supply of the upper gate drive circuit requires a floating power supply. For example, if the power is supplied by capacitor which composed in a bootstrapped circuit, care should be taken not to drop the voltage of the capacitor below UVLO threshold ( $V_{UVLO}$ ) due to the consumption of the gate drive circuit.

TLP5231 monitors the voltage of both positive ( $V_{CC2} - V_E$ ) and negative power supplies ( $V_E - V_{EE}$ ) on the secondary side. If the voltage is lower than UVLO threshold, it stops the gate output. When the positive power supply voltage exceeds UVLO threshold and the negative power supply voltage also exceeds UVLO threshold, it outputs the gate voltage. UVLO takes precedence over all functions then TLP5231 starts operating after releasing UVLO.

Consider the power supply voltage shown in Fig. 4.8 when the LED input signal is High. In this situation, the positive power supply ( $V_{CC2} - V_E$ ) has exceeded UVLO threshold  $V_{UVLOP+}$  first, but the negative power supply ( $V_E - V_{EE}$ ) has not exceeded UVLO threshold  $V_{UVLO-N+}$ . Therefore, FAULT is turned High to inform the primary side of an error.


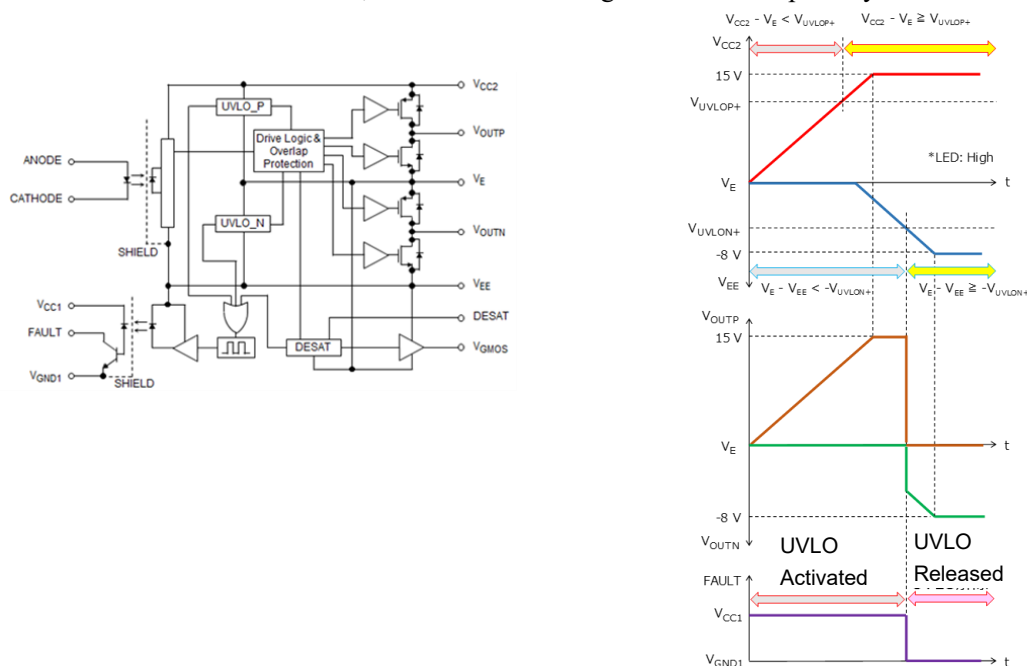


Fig. 4.8 Relationship between power supply voltage and  $V_{OUTP}$ ,  $V_{OUTN}$ , FAULT output

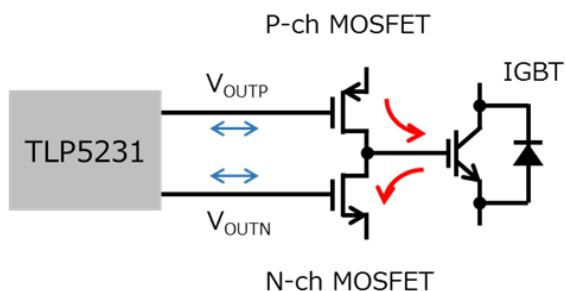




The dual-output type (Fig. 5.2.a) drives the P/N channel MOSFET separately, allowing full swing operation of the gate voltage of the power device.



High-side: P-ch MOSFET  
Low-side: N-ch MOSFET  
→ Full swing gate operation is **possible**

**Fig. 5.2.a Dual-Output Gate Driver**

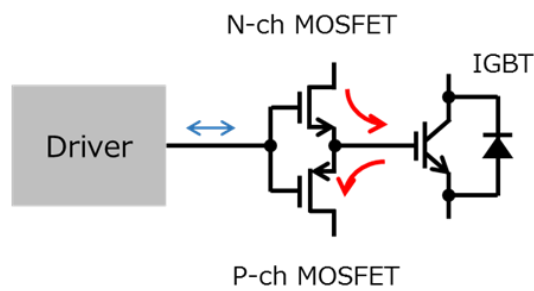

High-side: N-ch MOSFET  
Low-side: P-ch MOSFET  
→ Full swing gate operation is **impossible**

**Fig. 5.2.b Single-Output Gate Driver**

We also offer single-output smart gate driver coupler TLP5214A. Table 5 compares TLP5214A and TLP5231 features. Fig. 5.3 also shows the difference between the peripheral circuits.

**Table 5 Differences between TLP5231 and TLP5214A functions**

| Comparison term                       | TLP5231                                                                                                                        | TLP5214A                                                          |
|---------------------------------------|--------------------------------------------------------------------------------------------------------------------------------|-------------------------------------------------------------------|
| Secondary side output                 | <b>Dual output (negative logic)</b><br>*External P/N-channel MOSFET drive                                                      | Single output (positive logic)                                    |
| Power supply voltage (secondary side) | <b>Three rails: <math>V_{CC2}</math> (Positive Power), <math>V_E</math> (Common), and <math>V_{EE}</math> (Negative Power)</b> | Two rails of $V_{CC2}$ , $V_{EE}$<br>(available in $V_{EE}=V_E$ ) |
| Output peak current (max)             | $\pm 2.5$ A                                                                                                                    | $\pm 4.0$ A                                                       |
| Active Timing Control (Note 1)        | External P/N Channel MOSFET<br>Simultaneous ON prevention                                                                      | -                                                                 |
| Power element desaturation detection  | Built-in (Detect between $DESAT-V_E$ )                                                                                         | Built-in (Detect between $DESAT-V_E$ )                            |
| Soft turn-off                         | <b>Controllable (external)</b>                                                                                                 | Fixed (built-in)                                                  |
| UVLO function                         | For positive/negative power supply<br>Two UVLO circuits for $V_{CC2}$ and $V_{EE}$ based on $V_E$                              | For positive power supply only<br>( $V_E$ reference $V_{CC2}$ )   |
| Mute time (Protected) (Note 2)        | 0.68 to 1.7 ms                                                                                                                 | 7 $\mu$ s (minimum)                                               |
| Feedback function                     | When $V_{CE(sat)}$ desaturation is detected<br><b>UVLO status</b>                                                              | When $V_{CE(sat)}$ desaturation is detected                       |

(Note 1) Active timing control: Control is performed so that the external P-channel and N-channel MOSFET do not turn ON simultaneously. Control is performed so that the P channel MOSFET is turned on after the N channel MOSFET is turned off, and the N channel MOSFET is turned on after the P channel MOSFET is turned off.

(Note 2) Mute time: When the protection function is activated, the input LED signal is not accepted for a certain period of time. During this time, the protection operation is maintained.

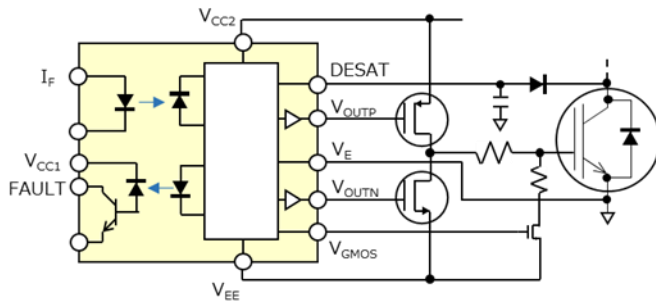


Fig. 5.3. a TLP5231 Peripheral Circuits


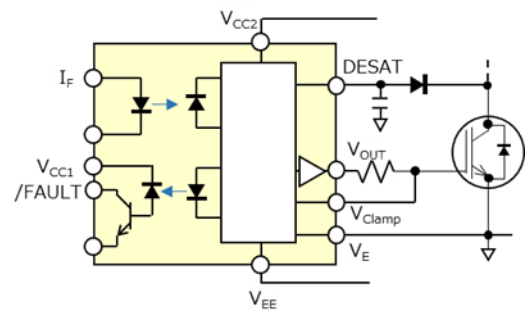



Fig. 5.3. b TLP5214A Peripheral Circuits

### 5.2. Comparison of TLP5231 and Single-Function Gate Driver Internal Structure

TLP5231 and single-function gate driver, which are optically isolated, the light-emitting diode chip and light-receiving IC chip are sealed with epoxy-resin. And the insulation distance of 0.4mm is guaranteed in order to provide reliable isolation. It can meet safety standards for a wide range of applications, from industrial equipment to various IT equipment.

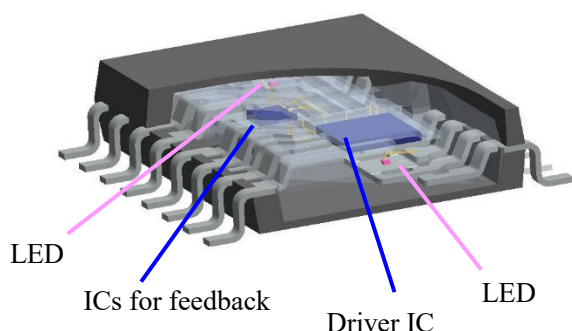

**Fig. 5.4.a Smart Gate Driver Coupler Internal Structure**

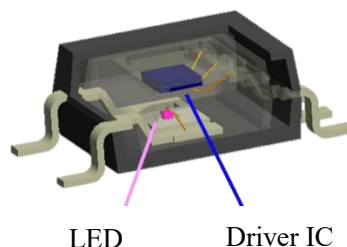


**Fig. 5.4.b Single-Function Gate Driver Coupler Internal Structure**

The smart gate driver coupler optically couples the driver IC that includes peripheral circuit, and feedback IC to the LED, as shown in Fig. 5.4.a. On the other hand, the protective function of the single-function gate driver coupler is only UVLO function described in Section 4, and the internal structure is also simple as shown in Fig. 5.4.b. Therefore, the protection function as a system must be designed separately from the gate driver, if necessary.

### 5.3. Derating of Dead-time Design

TLP5231 has two output lines for controlling MOSFET buffers Q1 and Q2, and provides a time difference (non-overlapping time) between ON/OFF signals of Q1 and Q2 to ensure dead time when both Q1 and Q2 are turned off. This eliminates the need for dead-time design, which was difficult with the buffer configuration in bipolar transistors, and prevents switching loss in simultaneous on-state generation.

- P-/N-channel Complementary-Dual-output with built-in active timing control suitable for driving buffer MOSFET.
- Buffer MOSFET dead-time designs are much easier, helping to reduce switching losses.

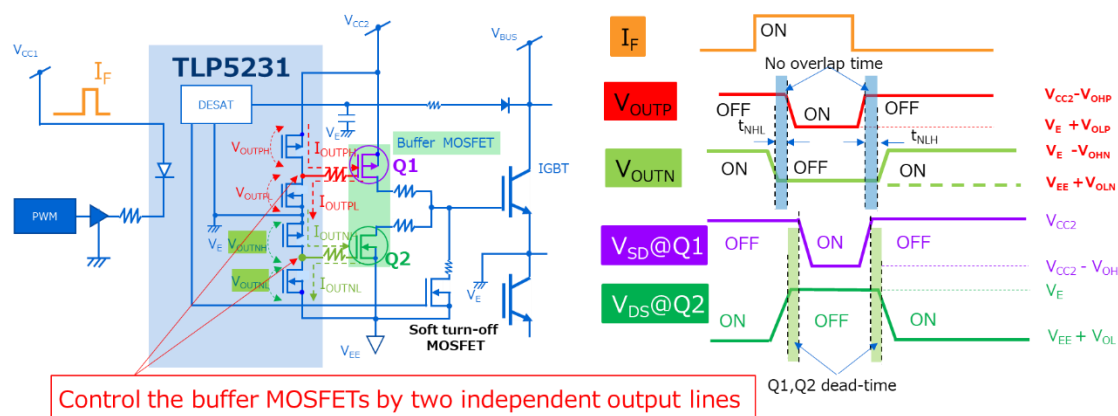

**Fig. 5.5 Timing image of dead time**



### 6. Example of Circuit Design Using TLP5231


#### 6.1. Example of Inverter Application Circuit

Fig. 6.1 shows an example of inverter application circuit of TLP5231. Although there are three phases of U, V, and W, the circuit configuration is common to all phases, so the U phase is shown as a representative in Fig. 6.1.b and Fig. 6.1.c. Table 6.1 shows the output specifications of this circuit example.

**Table 6.1 Output Specifications**

|                                     |    |     |
|-------------------------------------|----|-----|
| Positive Power Supply ( $V_{CC2}$ ) | 15 | V   |
| Negative Power Supply ( $V_{EE}$ )  | -8 | V   |
| Drive frequency                     | 20 | kHz |

※ The drive frequency is affected by the wiring length connected to the motor. Check and adjust the frequency on the final product.

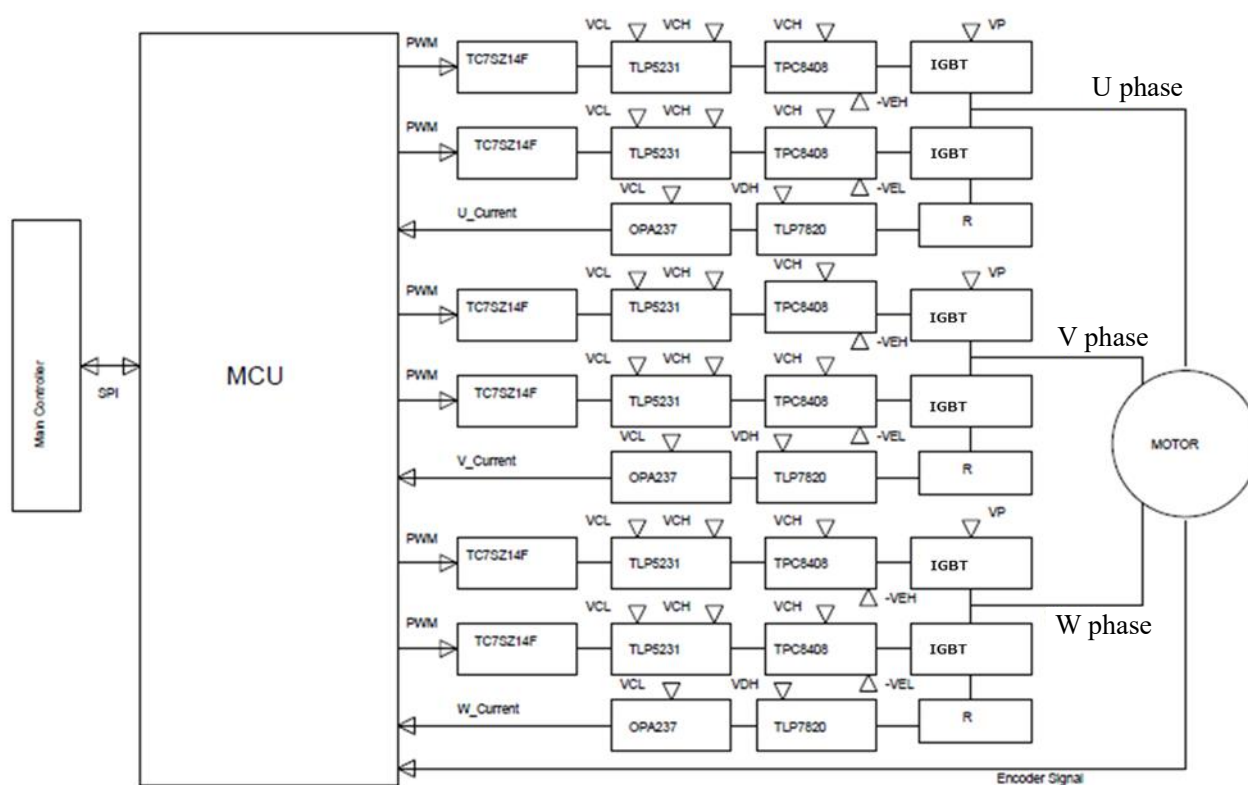

**Fig. 6.1.a TLP5231 Inverter Application Block Diagram**

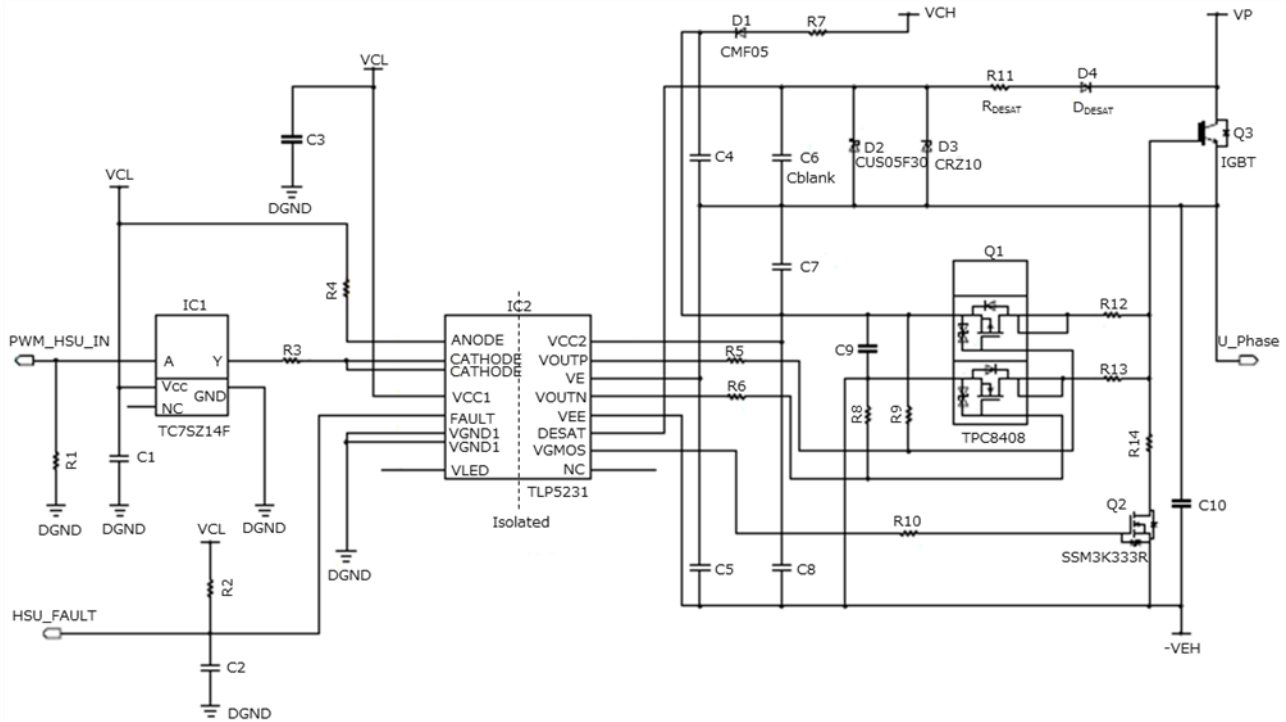


Fig. 6.1.b TLP5231 Inverter Application U-Phase (High Side)

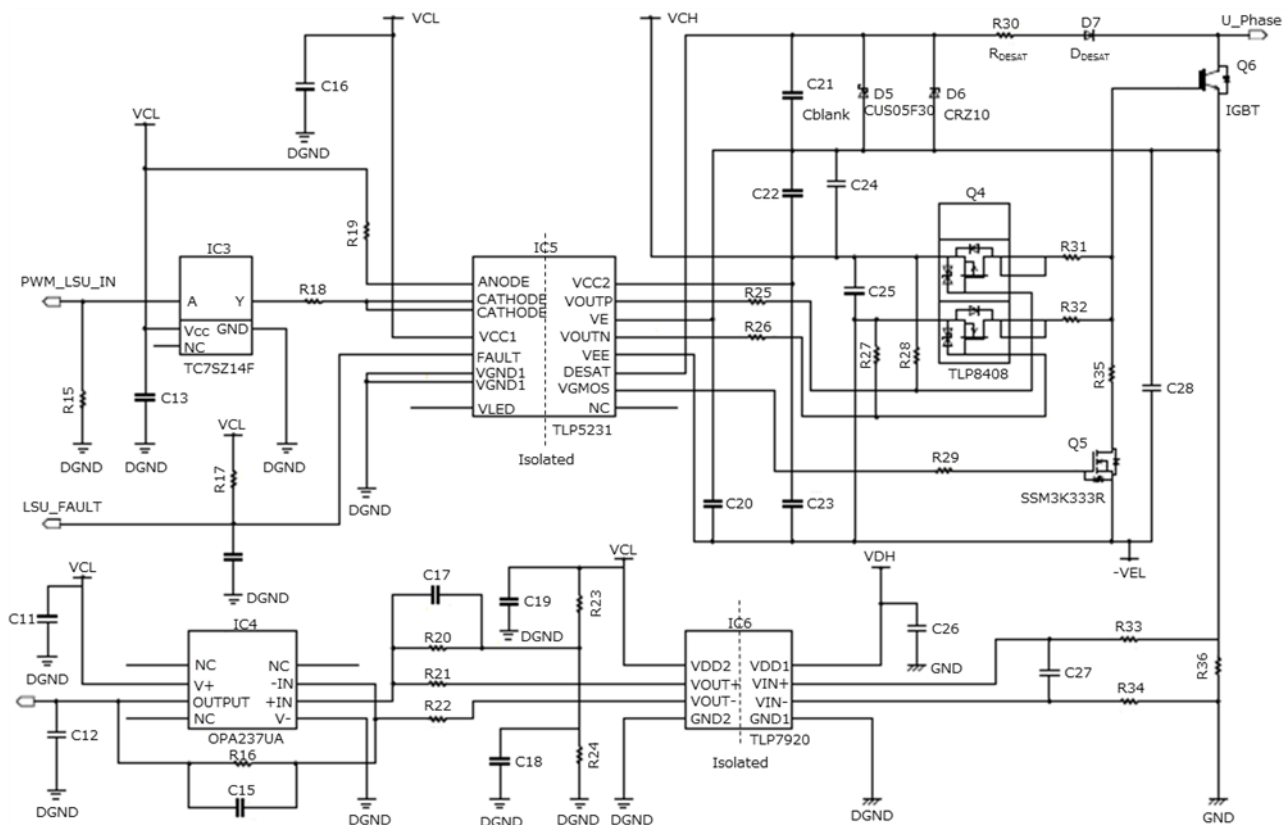


Fig. 6.1.c TLP5231 Inverter Application U-phase (Low Side)

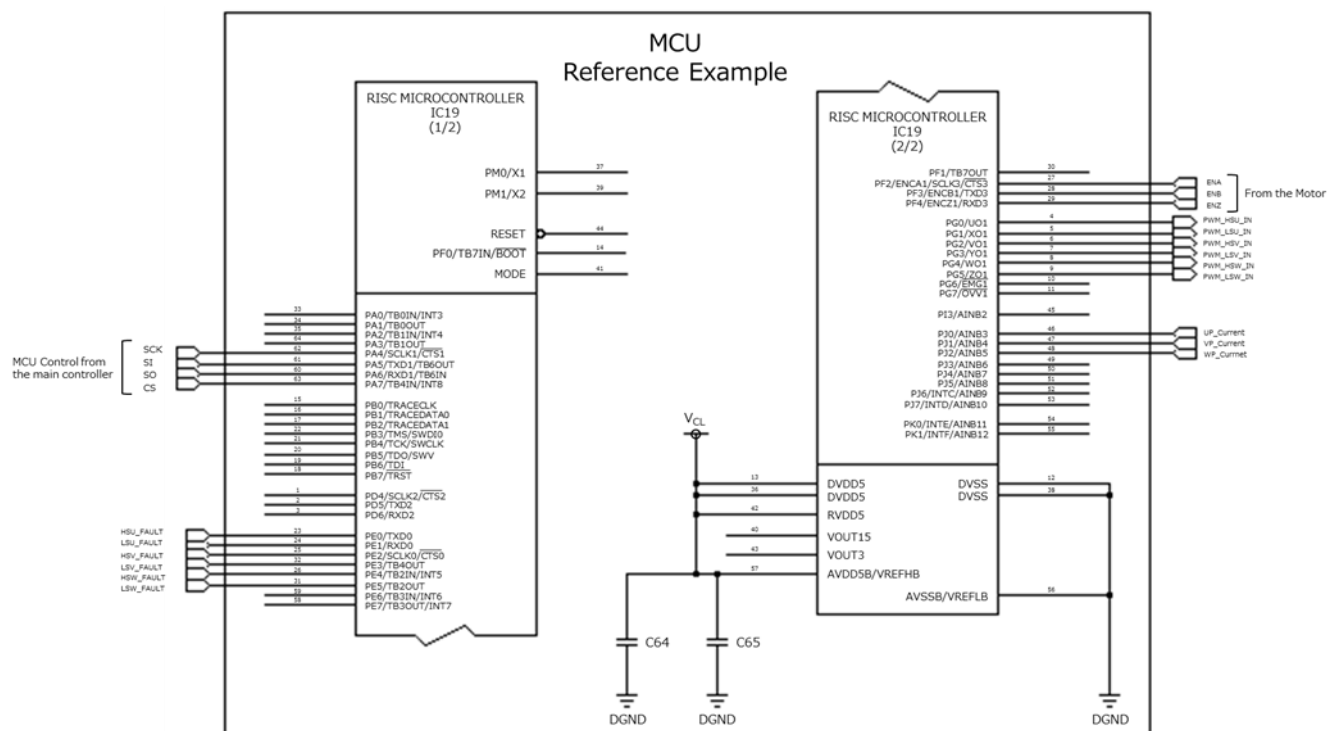


Fig. 6.1.d Typical MCU for TLP5231 Inverter Application

## 6.2. Selection of external MOSFET

The selection of the output current rating  $I_{pw\_charge}$  of the external buffer MOSFET (Ext-PMOS, Ext-NMOS) for power device gate drive is calculated by the gate charge  $Q_g$  and charge-time  $t_{pw\_charge}$  required to drive the power device.

$$I_{pw\_charge} = \frac{Q_g}{t_{pw\_charge}}$$

Consider driving IGBT of 1200V/600A. If  $Q_g$  is 3500 nC and the charge duration is 500 ns,

$$I_{pw\_charge} = \frac{3500nC}{500ns} = 7A$$

The peak current shall be about twice this value. Table 6.2 shows an example of selecting an external buffer MOSFET size and a MOSFET size for soft turn-off according to the power device you want to drive. Note that the withstand voltage of these MOSFET can be selected accordingly to the power supply voltage  $|V_{CC2}-V_{EE}|$ .

Table 6.2 External MOSFET Selection

| Part number in the circuit diagram | Q3/Q6                        | Q1/Q4    |          | Q2/Q5   |
|------------------------------------|------------------------------|----------|----------|---------|
| Power device                       | IGBT                         | Ext-PMOS | Ext-NMOS | GMOS    |
| Pattern 1                          | 600V/ 50A ( $Q_g=300nC$ )    | -2A(DC)  | 2A(DC)   | 2A(DC)  |
| Pattern 2                          | 1200V/ 200A ( $Q_g=2000nC$ ) | -5A(DC)  | 5A(DC)   | 5A(DC)  |
| Pattern 3                          | 1200V/ 600A ( $Q_g=3500nC$ ) | -10A(DC) | 10A(DC)  | 10A(DC) |



### 6.3. Selection of MOSFET for Soft Turn-off and Setting of Soft Turn-off Time

Use an external MOSFET(GMOS) to slowly shut off the gate after the short circuit of the power device ( $V_{CE(sat)}$ ) is detected by DESAT terminal. Slowly turning off the gate suppresses the spike-voltage ( $=|L \cdot di/dt|$ ) caused by the parasitic inductance of the wire so as not to destroy the power device.

Since the power device gate charge must be pulled out, it is recommended to use an N-channel MOSFET with a gate voltage/drain current rating equivalent to that of Ext-NMOS as shown in Table 6.2 for the rating of MOSFET(GMOS) for soft turn-off.

The gate-voltage  $V_G$  of the power elements decreases exponentially with time, as shown in the following equation.


$$V_G = (V_{CC2} + |V_{EE}|) \times \exp\left(\frac{-t}{C_{in} \times R_s}\right) - |V_{EE}|$$

Here,

t: Time,  $C_{in}$ : input capacitance of the power device,  $R_s$ : resistance between the gate of the power device and soft turn-off MOSFET

However, since the output voltage of the external buffer MOSFET is a full-swing operation, the default value is the power supply voltage, and  $R_{DS(on)}$  of GMOS is sufficiently small to be ignored.

When  $C_{in}=40\text{nF}$ ,  $R_s=180\Omega$ ,  $V_{CC2}=15\text{V}$ ,  $V_{EE}=-8\text{V}$ ,  $V_G$  changes as shown in Fig. 6.2.

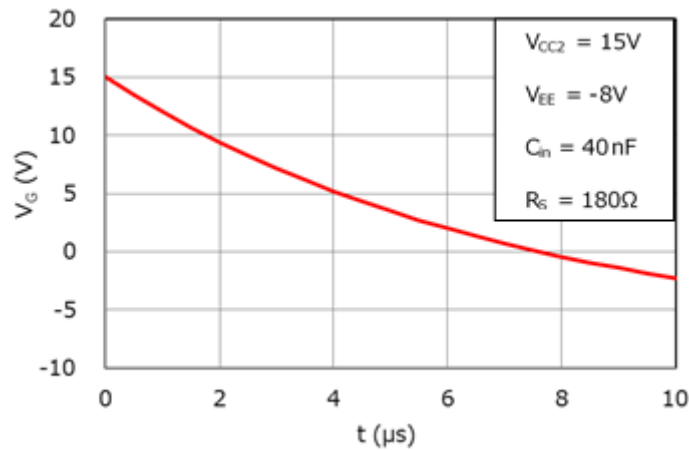

**Fig. 6.2 Example of gate voltage change of power devices (soft turn-off)**

If, for example,  $V_G$  is sufficiently lower than  $V_{th}$  of the power device and the time to drop to 2V is set to the soft turn-off time  $t_{STO}$ , the above equation is transformed,

$$t_{STO} = -C_{in} \times R_s \times \ln\left(\frac{2 + |V_{EE}|}{V_{CC2} + |V_{EE}|}\right) = -40\text{nF} \times 180\Omega \times \ln\left(\frac{2 + |-8\text{V}|}{15\text{V} + |-8\text{V}|}\right) \approx 6.0\mu\text{s}$$

And  $t_{STO}$  can be calculated.

### 6.4. Setting the blanking capacitor charge current and DESAT detect voltage

DESAT monitoring circuit based on the blanking capacitor charge current  $I_{CHG}$  is calculated as follows.

If IGBT is taken as GT40QR21 and the designed collector current is taken as 20A,  $V_{CE(SAT)}$  is estimated to be approximately 1.8 V from  $V_{GE}=15V$  curve in the Fig. 6.3. Note that  $V_{GE}=15V$  curve is selected as the minimum-gate design-voltage for typical IGBT. If  $V_F$  of DESAT Diode  $D_{DESAT}$  is 2.4V and  $I_{CHG}$  from DESAT terminal of TLP5231 is 540 $\mu$ A,  $R_{DESAT}$  is 3 k ohms, the voltage drops at DESAT terminal and  $V_E$  terminal (IGBT emitter potential) is:

$$\begin{aligned} V_{DESAT(ON)} &= V_{CE(SAT)} + V_{F(DDESAT)} + (R_{DESAT} \times I_{CHG}) \\ &= 1.8 \text{ V} + 2.4 \text{ V} + (3000\Omega \times 540\mu\text{A}) = 5.82 \text{ V} \end{aligned}$$

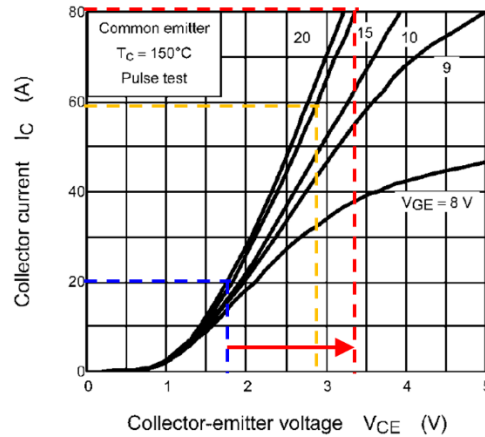


Fig. 6.3 Characteristic curve of  $I_C$ - $V_{CE}$  in IGBT (GT40QR21)

If a short circuit occurs for some reason and the current flowing through IGBT increases along the static characteristics curve,  $V_{DESAT(ON)}$  increases from 5.82V.

When this  $V_{DESAT(ON)}$  exceeds 7.5V (min), TLP5231 judges it as abnormal and activates the protective function.

For  $V_{CE}$  of GT40QR21 at this time,

$$\begin{aligned} V_{CE(SAT)} &= V_{DESAT(ON)} - V_{F(DDESAT)} - (R_{DESAT} \times I_{CHG}) \\ &= 7.5\text{V} - 2.4\text{V} - 1.62\text{V} = 3.48\text{V} \end{aligned}$$

Therefore, after the collector current exceeds 80A from the static characteristic curve, it is recognized as a DESAT state and enters the protective operation.

### 6.5. Setting the Blanking Capacitor ( $C_{BLANK}$ )

Section 4.3 explains how to set the blanking time  $t_{BLANK}$  shorter than IGBT short-circuit tolerance  $t_{SC}$ .

$t_{BLANK}$  between the start of  $C_{BLANK}$  charging and the start of the protective operation is calculated from the saturation voltage  $V_{CE(sat)}$  of IGBT and the forward voltage  $V_F$  of DESAT Diode and the voltage drop of  $R_{DESAT}$ .

$$t_{BLANK} = \{C_{BLANK} \times (V_{DESAT(ON)} - (V_{CE(sat)} + V_F + I_{CHG} \times R_{DESAT}))\} / I_{CHG}$$

Note that  $t_{BLANK}$  must be shorter than IGBT short-circuit tolerance  $t_{sc}$  along with the soft shutdown duration.

Referring to the case from the previous session, assuming that  $C_{BLANK}$  is 100pF

$$\begin{aligned} t_{BLANK} &= \{C_{BLANK} \times (V_{DESAT(ON)} - (V_{CE(sat)} + V_F + I_{CHG} \times R_{DESAT}))\} / I_{CHG} \\ &= \{100\text{pF} \times (7.5\text{V} - (1.8\text{V} + 2.4\text{V} + 540\mu\text{A} \times 3\text{k}\Omega))\} / 540\mu\text{A} \\ &= \{100\text{pF} \times (7.5\text{V} - 5.82\text{V})\} / 540\mu\text{A} = 0.31\mu\text{s} \end{aligned}$$

Since it is less than 1  $\mu$ s, if the short-circuit tolerance is 5 $\mu$ s or more, there is no problem. For example, if  $C_{BLANK}$  is changed to 500pF and  $V_F$  is reduced to 1V for enhancing anti-noise measures,

$$\begin{aligned} &\{500\text{pF} \times (7.5\text{V} - (1.8\text{V} + 1.0\text{V} + 540\mu\text{A} \times 3\text{k}\Omega))\} / 540\mu\text{A} \\ &= \{500\text{pF} \times (7.5\text{V} - 4.42\text{V})\} / 540\mu\text{A} = 2.85\mu\text{s} \end{aligned}$$

As it will be delayed above, care must be taken when designing.

### 7. Example of Operation Waveforms Using TLP5231

Using the power device shown in Table 7.1, external buffer MOSFET, and soft turn-off MOSFET, the circuit shown in Fig. 7.1 was used to evaluate the double-pulse operation. Double-pulse testing is a widely used technique for evaluating the switching properties of power devices such as MOSFET and IGBT. This time, we conducted a double-pulse test using TLP5231 as gate driver, and confirmed the switching waveform of IGBT. The circuit of the evaluation board is shown in Fig. 7.2, and the constant setting is shown in Table 7.2.

Table 7.1 Device used for operation test

| Power device<br>IGBT                                               | Buffer MOSFET                 |                            | MOSFET for soft turn-off<br>GMOS |
|--------------------------------------------------------------------|-------------------------------|----------------------------|----------------------------------|
|                                                                    | Ext-PMOS                      | Ext-NMOS                   |                                  |
| IGBT Module Made by Fuji Electric<br>7MBR150XRE120-50(1200V/ 150A) | TPC8407<br>$I_{D(MAX)}=-7.4A$ | TPC8407<br>$I_{D(MAX)}=9A$ | SSM3K333R<br>$I_{D(MAX)}=6A$     |

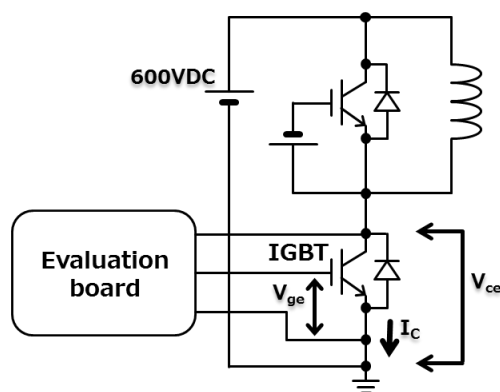


Fig. 7.1 Normal operation check circuit


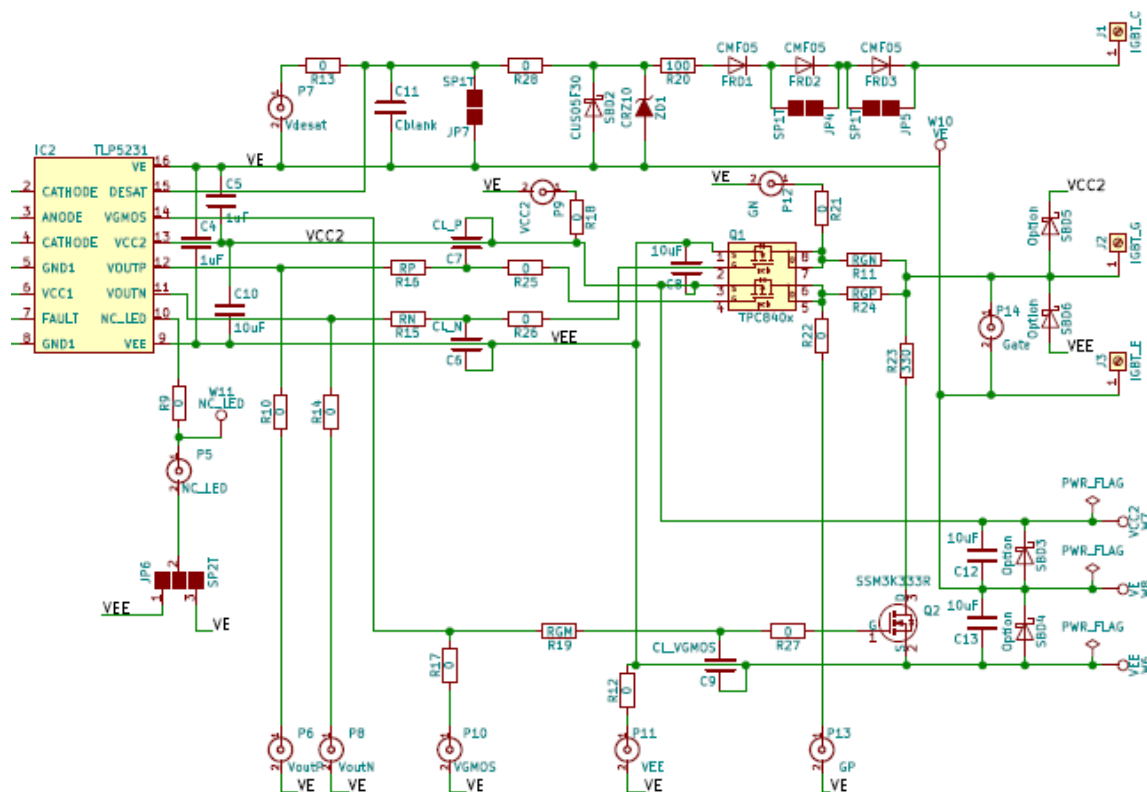


Fig. 7.2 Evaluation Board Circuit

**Table 7.2 TLP5231 Evaluation board constant setting**


| Type                       | Part code        | Constant | Unit | Remarks                                 |
|----------------------------|------------------|----------|------|-----------------------------------------|
| Gate Positive Power Supply | V <sub>CC2</sub> | 15V      | V    | IGBT Positive Gate Supply Voltage       |
| Gate negative power supply | V <sub>EE</sub>  | -15V     | V    | IGBT Negative Gate Power Supply Voltage |
| Resistance                 | R16              | 4.7      | Ω    | Buffer input resistor (P side) RP       |
| Resistance                 | R15              | 4.7      | Ω    | Buffer input resistor (N side) RN       |
| Resistance                 | R24              | 20       | Ω    | Gate resistor RGP for IGBT on           |
| Resistance                 | R11              | 10       | Ω    | Gate resistor RGN for IGBT off          |
| Resistance                 | R19              | 10       | Ω    | MOSFET gate resistor for soft turn-off  |
| Resistance                 | R23              | 330      | Ω    | Gate resistor for IGBT soft turn-off    |
| Resistance                 | R20              | 100      | Ω    | DESAT resistor                          |
| Capacitor                  | C11              | 100      | pF   | Blanking capacitor                      |
| Diode                      | FRD1             | 1000     | V    | CMF05(VRRM:1000V)                       |
| Diode                      | FRD2             | 1000     | V    | CMF05(VRRM:1000V)                       |

Fig. 7.3 below shows the overall waveform of normal operation. Fig. 7.4 and Fig. 7.5 show the enlarged waveforms of the red frames (b) and (c).

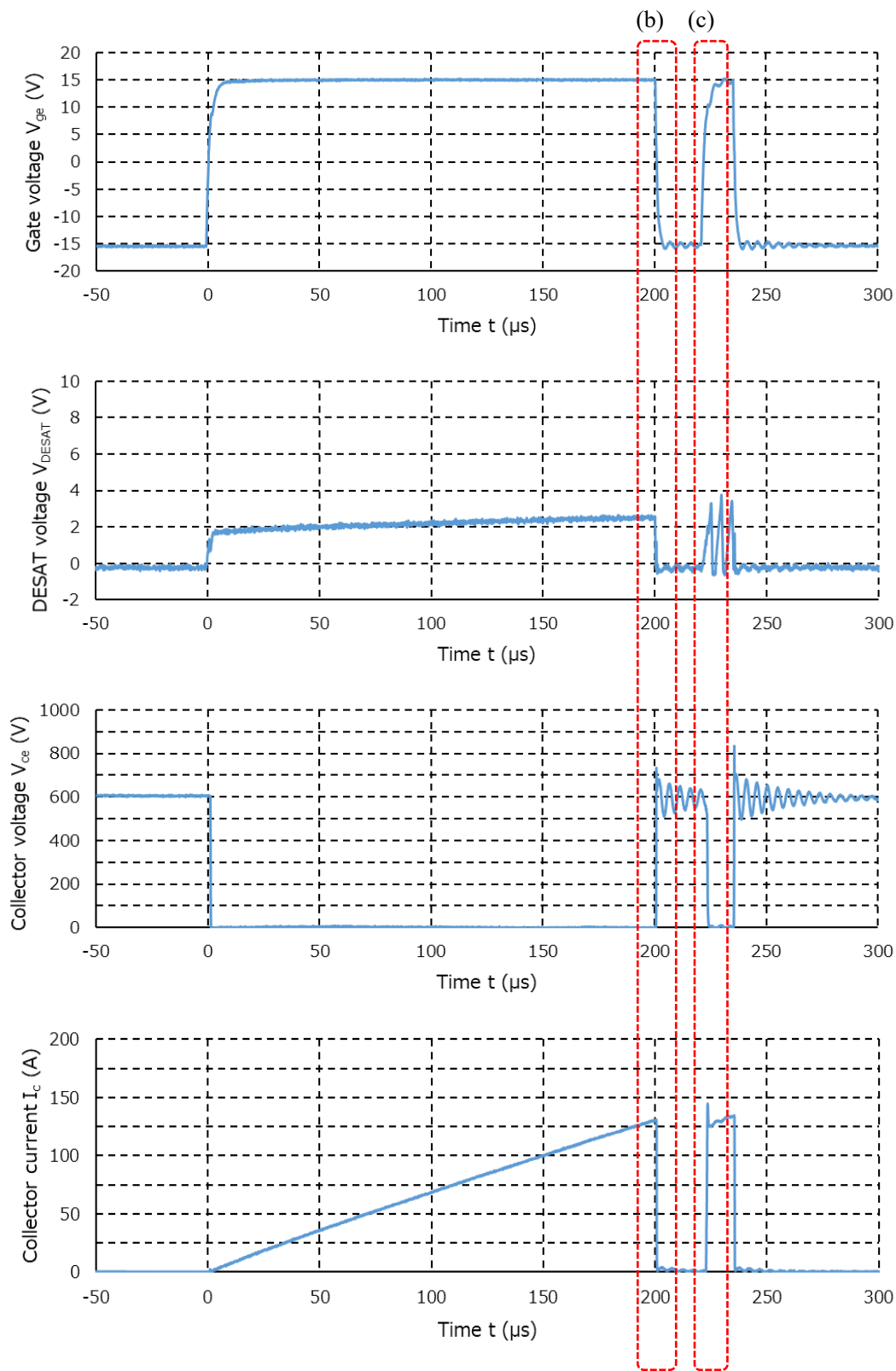

**Fig. 7.3 Overall waveform of normal switching operation (a)**


Fig. 7.4 below shows an enlarged waveform of the red frame (b).

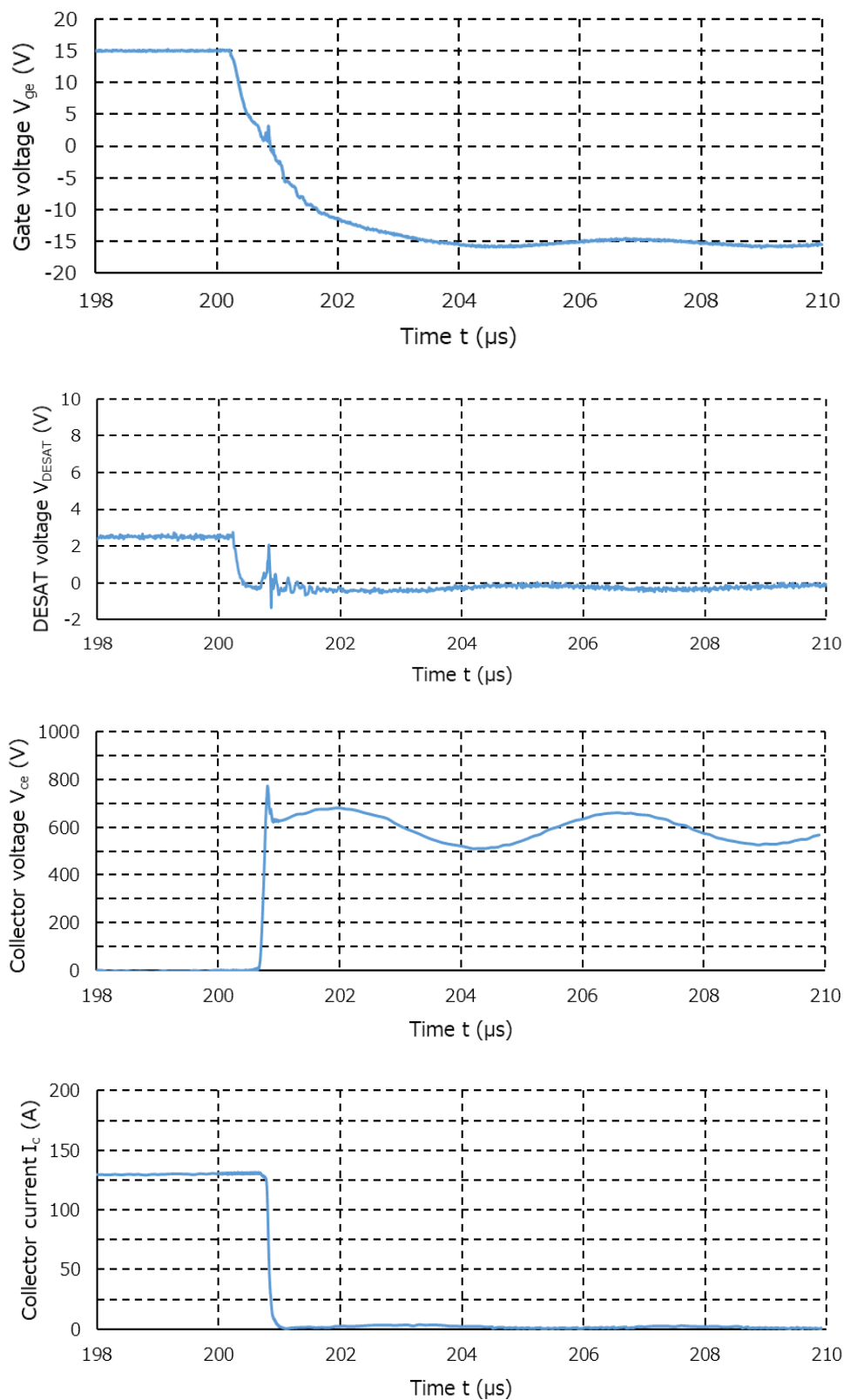

**Fig. 7.4 Enlarged waveform (b)**

**Normal switching operation turn-off**


Fig. 7.5 below shows a waveform obtained by enlarging the red frame (c) described above. No particular problems are found, and you can confirm that TLP5231 correctly drives the gate.

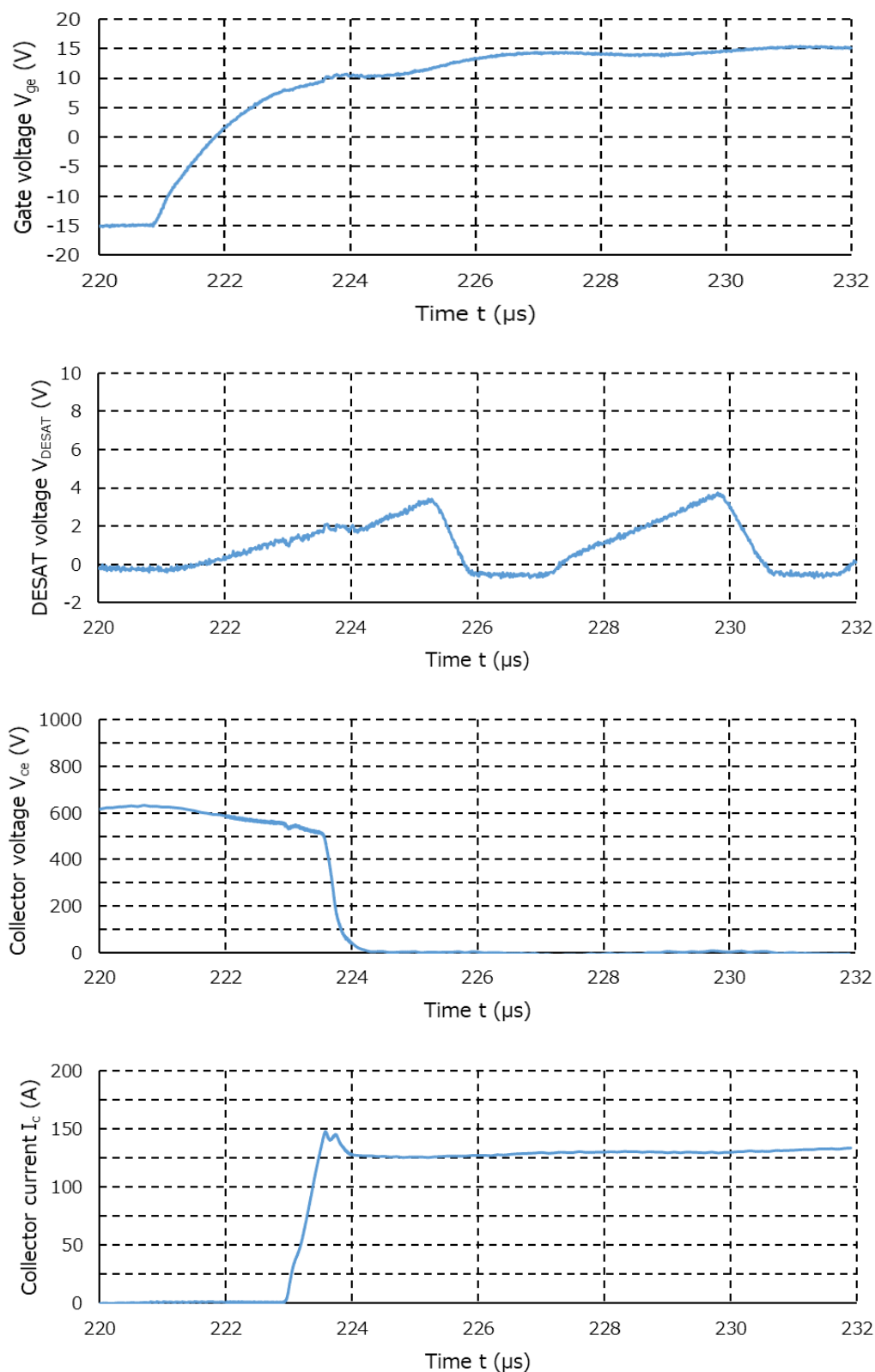


**Fig. 7.5 Enlarged waveform (c)**

**Normal switching operation turn-on**

We then verified the operation of IGBT short-circuit by the circuit shown in Fig. 7.6. Fig. 7.7 shows the verification waveform. Soft turn-off starts about 5 $\mu$ s after the short-circuit current flows, and it can be confirmed that the short-circuit protection operates normally without destruction of IGBT.

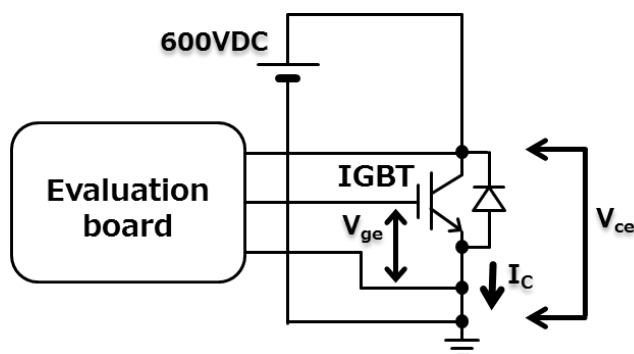

**Fig. 7.6 IGBT Short-Circuit Protection Validation Circuit**

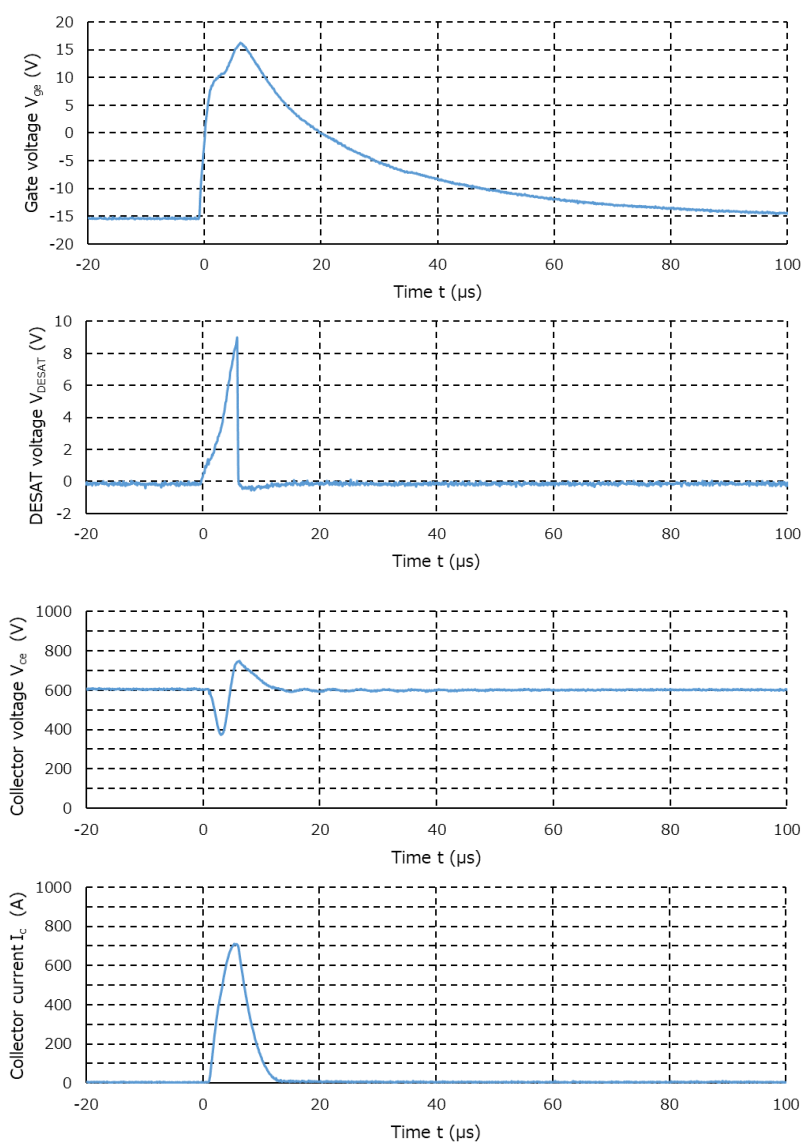

**Fig. 7.7 IGBT Short-Circuit Protection Operation Waveform**



**Changelog**

| <b>Version<br/>information</b> | <b>Date</b> | <b>Content of change</b> |
|--------------------------------|-------------|--------------------------|
| Rev. 1.0                       | 2021-10-28  | First edition            |

## Precautions for handling the product

Toshiba Corporation and its subsidiaries and affiliates are collectively referred to as "TOSHIBA".  
Hardware, software and systems described in this document are collectively referred to as "Product".

- TOSHIBA reserves the right to make changes to the information in this document and related Product without notice.
- This document and any information herein may not be reproduced without prior written permission from TOSHIBA. Even with TOSHIBA's written permission, reproduction is permissible only if reproduction is without alteration/omission.
- Though TOSHIBA works continually to improve Product's quality and reliability, Product can malfunction or fail. Customers are responsible for complying with safety standards and for providing adequate designs and safeguards for their hardware, software and systems which minimize risk and avoid situations in which a malfunction or failure of Product could cause loss of human life, bodily injury or damage to property, including data loss or corruption. Before customers use the Product, create designs including the Product, or incorporate the Product into their own applications, customers must also refer to and comply with (a) the latest versions of all relevant TOSHIBA information, including without limitation, this document, the specifications, the data sheets and application notes for Product and the precautions and conditions set forth in the "TOSHIBA Semiconductor Reliability Handbook" and (b) the instructions for the application with which the Product will be used with or for. Customers are solely responsible for all aspects of their own product design or applications, including but not limited to (a) determining the appropriateness of the use of this Product in such design or applications; (b) evaluating and determining the applicability of any information contained in this document, or in charts, diagrams, programs, algorithms, sample application circuits, or any other referenced documents; and (c) validating all operating parameters for such designs and applications. **TOSHIBA ASSUMES NO LIABILITY FOR CUSTOMERS' PRODUCT DESIGN OR APPLICATIONS.**
- **PRODUCT IS NEITHER INTENDED NOR WARRANTED FOR USE IN EQUIPMENTS OR SYSTEMS THAT REQUIRE EXTRAORDINARILY HIGH LEVELS OF QUALITY AND/OR RELIABILITY, AND/OR A MALFUNCTION OR FAILURE OF WHICH MAY CAUSE LOSS OF HUMAN LIFE, BODILY INJURY, SERIOUS PROPERTY DAMAGE AND/OR SERIOUS PUBLIC IMPACT ("UNINTENDED USE").** Except for specific applications as expressly stated in this document, Unintended Use includes, without limitation, equipment used in nuclear facilities, equipment used in the aerospace industry, lifesaving and/or life supporting medical equipment, equipment used for automobiles, trains, ships and other transportation, traffic signaling equipment, equipment used to control combustions or explosions, safety devices, elevators and escalators, and devices related to power plant. **IF YOU USE PRODUCT FOR UNINTENDED USE, TOSHIBA ASSUMES NO LIABILITY FOR PRODUCT.** For details, please contact your TOSHIBA sales representative or contact us via our website.
- Do not disassemble, analyze, reverse-engineer, alter, modify, translate or copy Product, whether in whole or in part.
- Product shall not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable laws or regulations.
- The information contained herein is presented only as guidance for Product use. No responsibility is assumed by TOSHIBA for any infringement of patents or any other intellectual property rights of third parties that may result from the use of Product. No license to any intellectual property right is granted by this document, whether express or implied, by estoppel or otherwise.
- **ABSENT A WRITTEN SIGNED AGREEMENT, EXCEPT AS PROVIDED IN THE RELEVANT TERMS AND CONDITIONS OF SALE FOR PRODUCT, AND TO THE MAXIMUM EXTENT ALLOWABLE BY LAW, TOSHIBA (1) ASSUMES NO LIABILITY WHATSOEVER, INCLUDING WITHOUT LIMITATION, INDIRECT, CONSEQUENTIAL, SPECIAL, OR INCIDENTAL DAMAGES OR LOSS, INCLUDING WITHOUT LIMITATION, LOSS OF PROFITS, LOSS OF OPPORTUNITIES, BUSINESS INTERRUPTION AND LOSS OF DATA, AND (2) DISCLAIMS ANY AND ALL EXPRESS OR IMPLIED WARRANTIES AND CONDITIONS RELATED TO SALE, USE OF PRODUCT, OR INFORMATION, INCLUDING WARRANTIES OR CONDITIONS OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, ACCURACY OF INFORMATION, OR NONINFRINGEMENT.**
- GaAs (Gallium Arsenide) is used in Product. GaAs is harmful to humans if consumed or absorbed, whether in the form of dust or vapor. Handle with care and do not break, cut, crush, grind, dissolve chemically or otherwise expose GaAs in Product.
- Do not use or otherwise make available Product or related software or technology for any military purposes, including without limitation, for the design, development, use, stockpiling or manufacturing of nuclear, chemical, or biological weapons or missile technology products (mass destruction weapons). Product and related software and technology may be controlled under the applicable export laws and regulations including, without limitation, the Japanese Foreign Exchange and Foreign Trade Law and the U.S. Export Administration Regulations. Export and re-export of Product or related software or technology are strictly prohibited except in compliance with all applicable export laws and regulations.
- Please contact your TOSHIBA sales representative for details as to environmental matters such as the RoHS compatibility of Product. Please use Product in compliance with all applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive. **TOSHIBA ASSUMES NO LIABILITY FOR DAMAGES OR LOSSES OCCURRING AS A RESULT OF NONCOMPLIANCE WITH APPLICABLE LAWS AND REGULATIONS.**

**TOSHIBA ELECTRONIC DEVICES & STORAGE CORPORATION**  
<https://toshiba.semicon-storage.com/>